



Nagarjuna Degree College
38/36, Ramagondanahalli,
Yelahanka Hobli,
Bengaluru - 560 064.

11321

Reg. No.

--	--	--	--	--	--	--	--

III Semester B.Sc. Degree Examination, March/April - 2022

PHYSICS

Electricity and Magnetism

(CBCS Semester Scheme Repeaters 2018-19 and onwards prior to 2020)

Paper - III

Time : 3 Hours

Maximum Marks : 70

Instructions to candidates :

- 1) Answer any Five questions from each part.
- 2) Use of Non-Programmable scientific calculator is allowed.

PART-A

Answer any Five questions. Each question carries 8 marks. (5×8=40)

1. a) Distinguish between an ideal voltage source and an ideal current source.
b) State and prove superposition theorem. (2+6)
2. Derive an expression for the decay of current in a series LR circuit. Define time constant. Show the variation graphically. (8)
3. a) State and explain Biot-Savart's law.
b) Arrive at the expression for the magnetic field at any point on the axis of a current carrying solenoid. (3+5)
4. a) State and explain Ampere's circuital law.
b) Using Ampere's circuital law, deduce an expression for magnetic field at any point near an infinitely long straight wire carrying current. (4+4)
5. Derive Maxwell Electromagnetic equations $\nabla \cdot \vec{B} = 0$ and $\nabla \times \vec{E} = -\frac{\partial \vec{B}}{\partial t}$ (4+4)
6. Derive Maxwell's electromagnetic wave equation $\nabla^2 \vec{E} = \mu_0 \epsilon_0 \frac{\partial^2 \vec{E}}{\partial t^2}$ (8)

[P.T.O.]



7. What is resonance in a series LCR ac circuit? Arrive at the expression for its resonant frequency and current at resonance. (8)
8. a) State and explain the two laws of thermoelectricity.
b) Explain with a diagram the working of a thermopile. (4+4)


PART - B

Answer any Five questions. Each question carries 4 marks.

(5×4=20)

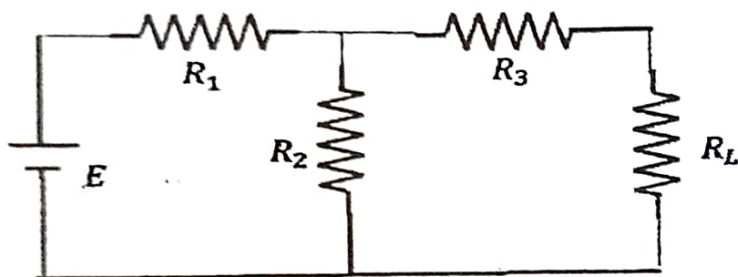9. Find the value of R_L required to obtain maximum power in the circuit shown.

$$R_1 = 300\Omega, R_2 = 100\Omega, R_3 = 25\Omega \text{ and } E = 100V$$



10. A coil having a resistance of $15\ \Omega$ and an inductance of $10\ \text{H}$ is connected to a $90\ \text{V}$ battery. Determine the value of current after $0.67\ \text{s}$.
11. An electron is approaching a straight wire carrying a current of $20\ \text{A}$ at a speed of $10^7\ \text{ms}^{-1}$. What is the force on the electron when it is at a distance of $0.02\ \text{m}$ from the wire?
12. A Helmholtz galvanometer has coils each of radius $0.2\ \text{m}$ and number of turns 100 . Calculate the current through the coils which produces a deflection of 45° . Given $B_H = 0.35 \times 10^{-4}\ \text{T}$.
13. Find the divergence of an electric field $\vec{E} = x^2z\hat{i} + 2y^2z^2\hat{j} + xy^2z\hat{k}$ at point $(1, -1, 1)$.
14. Determine the value of permittivity of free space using the value of speed of light in vacuum $= 3 \times 10^8\ \text{ms}^{-1}$ and permeability of free space $= 4\pi \times 10^{-7}\ \text{Hm}^{-1}$.
15. A $60\ \text{V}$, $10\ \text{W}$ lamp to be run on a $100\ \text{V}$, $60\ \text{Hz}$ ac mains. Calculate the inductance of the choke coil to be connected with the lamp.
16. Calculate the neutral temperature and temperature of inversion for a thermocouple between $0^\circ\ \text{C}$ and $100^\circ\ \text{C}$ for which Seebeck coefficients are $a = 20\ \mu\text{V}/^\circ\ \text{C}$ and $b = -0.05\ \mu\text{V}/^\circ\ \text{C}^2$.



PART - C

17. Answer any **Five** questions. Each question carries **2** marks.

(5×2=10)

- a) Self-inductance of a coil is called electrical inertia. Explain.
 - b) When does a dc LCR series circuit get critically damped?
 - c) An electrical charge is kept near a magnet. Will it experience force? Explain.
 - d) Why two coils are used in a Helmholtz galvanometer instead of single coil?
 - e) Is it possible to have only electric wave or magnetic wave propagating through space? Explain.
 - f) Displacement current is as real as conduction current. Explain.
 - g) Is power dissipated by a pure inductor? Justify.
 - h) Is Seebeck effect reversible? Explain.
-